

Issues with Implementing Transmitter Pre-Compensation

**Richard Uber
Quantum Corporation**


SCSI Physical Working Group Meeting

09 Feb 2000


Huntington Beach, CA

- **Amplitude sensitivity to common-mode voltage.**
- **Effects on driver Z_{out} and common-mode operating point.**
- **Feasibility of driving output stages harder.**
- **Feasibility of larger output stages.**
- **Slew rate issues.**
- **Effects on NEXT and FEXT.**
- **Power dissipation concerns.**
- **Power efficiency of a boost driver strategy.**

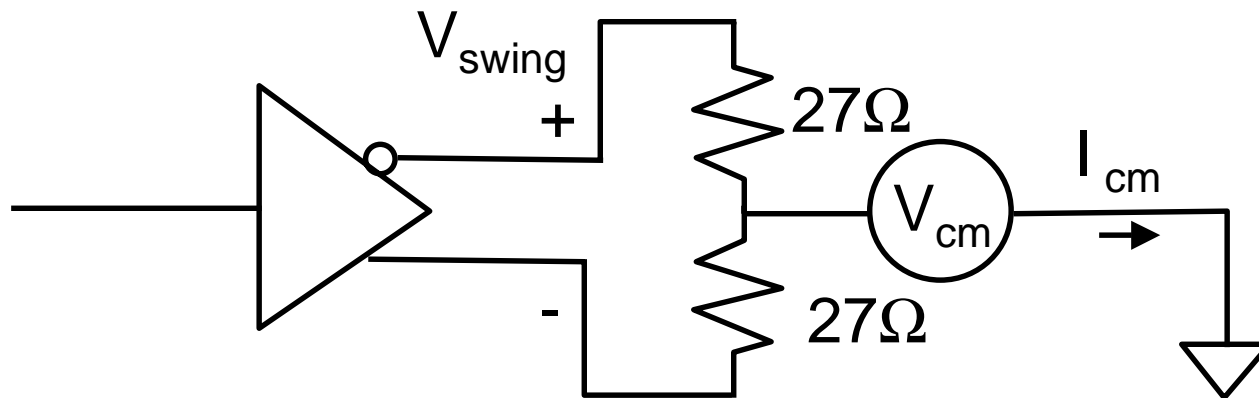- It's difficult to drive more current with existing current-mode drivers
- Simulation circuit for observing differential V_{swing} and I_{cm}
 - Without terminator, negation swings smaller by 115mV




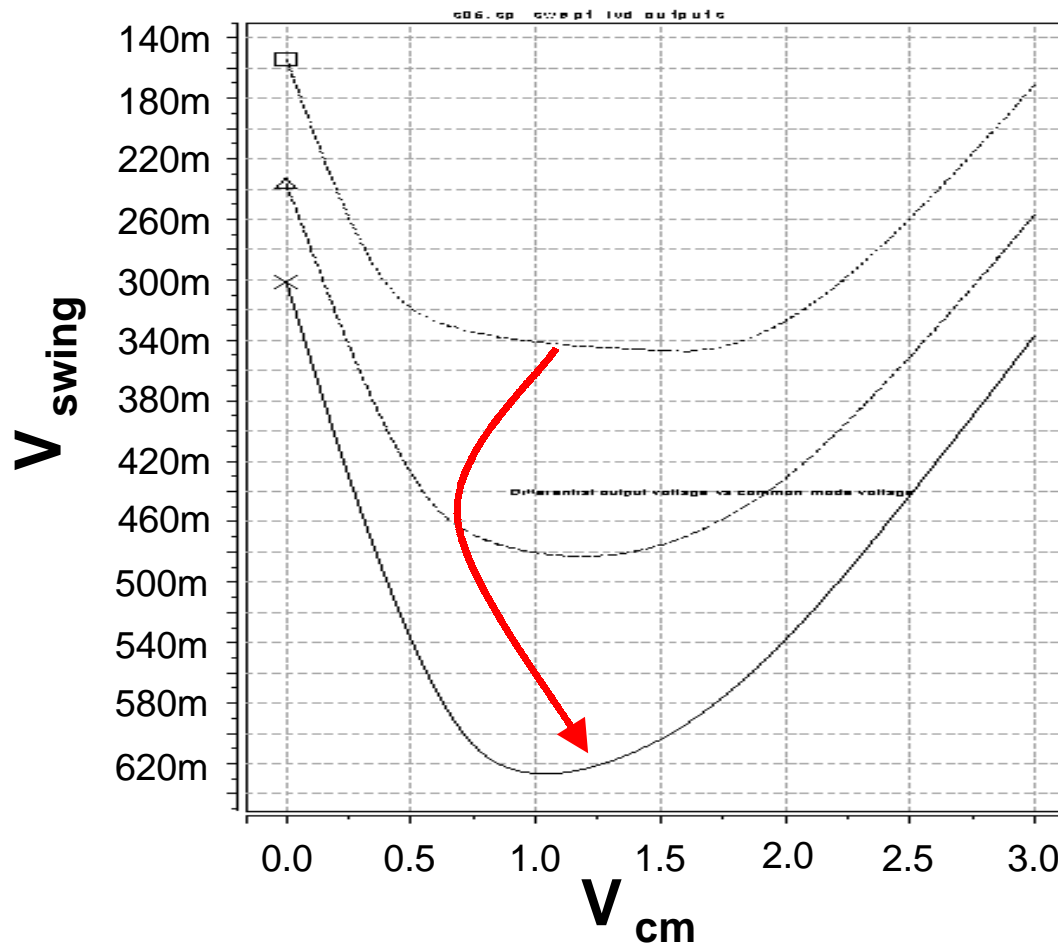- LVD V_{swing} for V_{cm} swept from 0V to 3.0V
- Currents are highly variable outside of the allowed common-mode range.



**Increased
driver
amplitude**

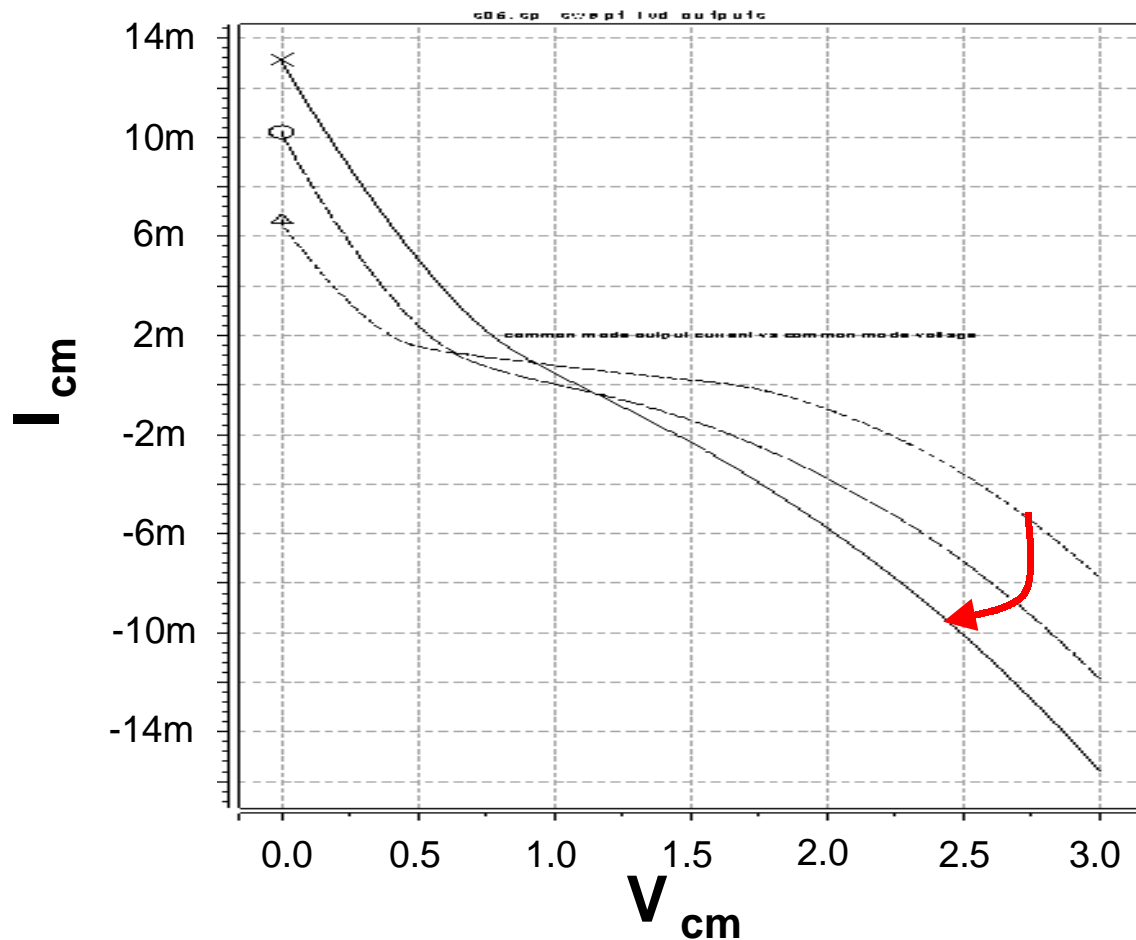
- LVD I_{cm} for V_{cm} swept from 0V to 3.0V
- Currents are highly variable outside of the allowed common-mode range




Increasing
driver
amplitude

- Usable range (0.855V - 1.645V) V_{swing} versus V_{cm}
- Linearity degrades with increasing signal amplitude

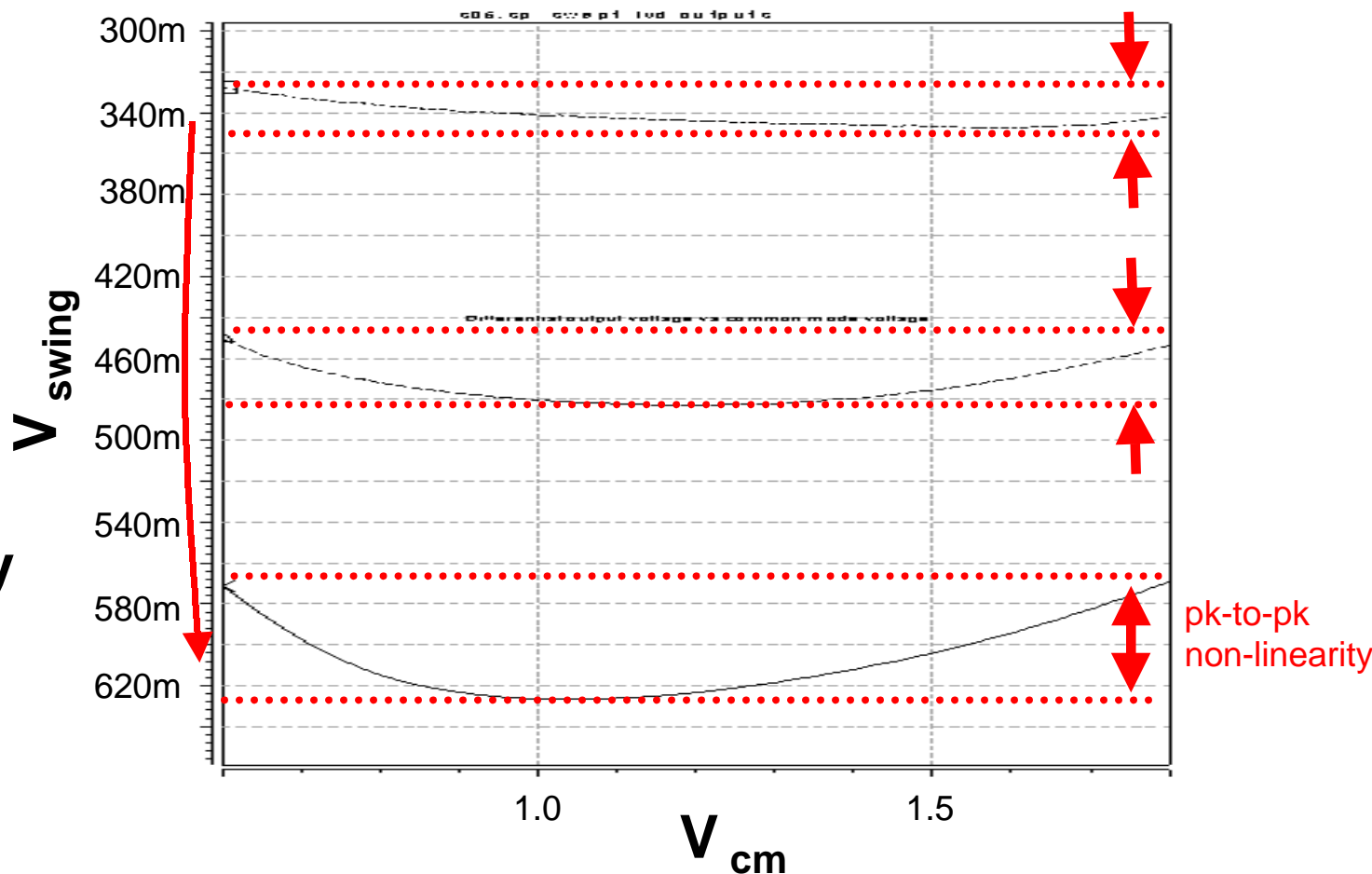Increasing driver amplitude
⇒
increases non-linearity



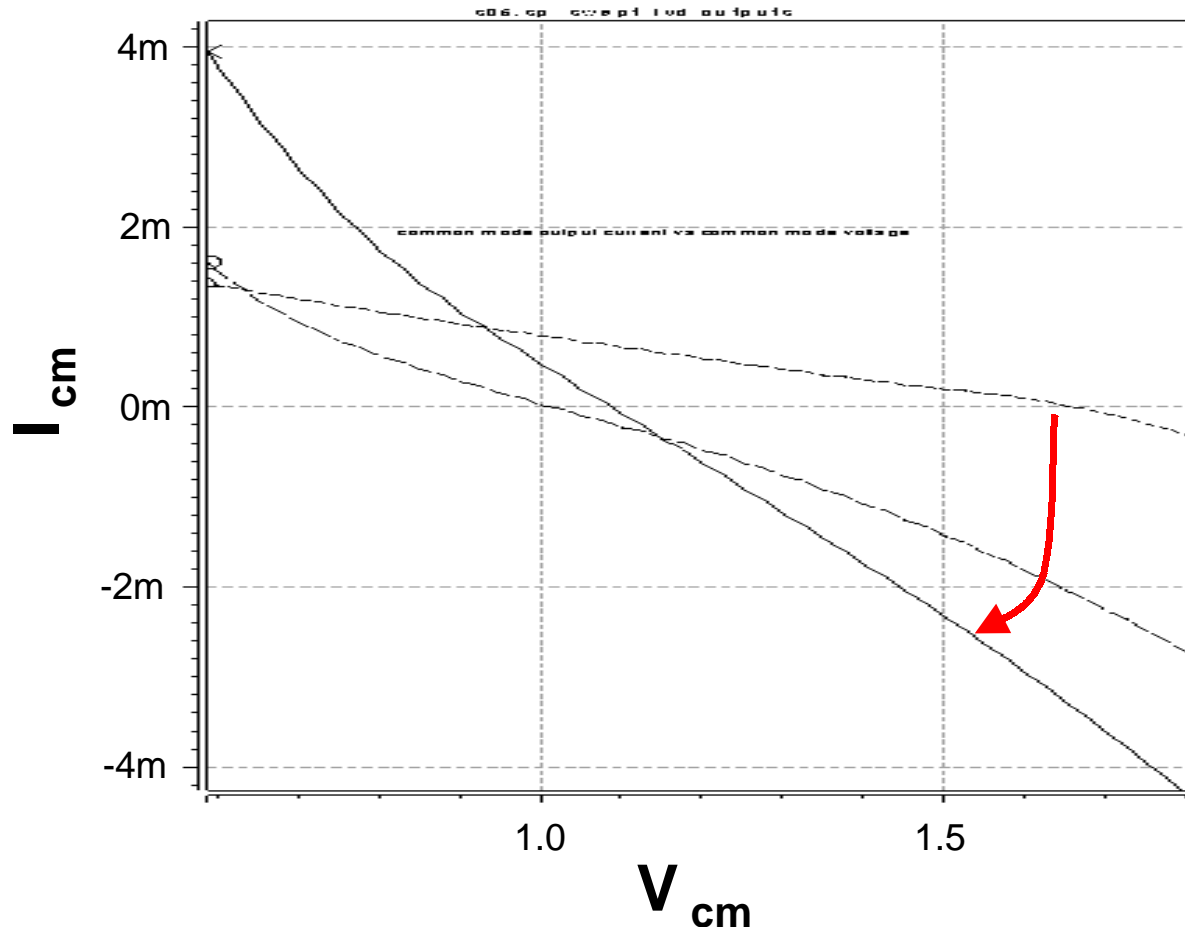- Usable range (0.855V - 1.645V) I_{cm} versus V_{cm}
- Linearity degrades with increasing signal amplitude




**Increasing
driver
amplitude**

- Differential V_{swing} becomes a strong function of V_{cm} .
- D.C. common-mode current increases (lower Z_{out} for LVD current mode driver).
- Current sources are more problematic.
- Common-mode noise from 3.3V supply increases.
- Turning on and off a “boost driver” will result in common-mode glitches during driver enable and disable.
- Turning on and off a “boost driver” will result in a high frequency common-mode pulses on the bus.

- Consider a 11001100 data pattern, on a driver with 1.0mA of common-mode mismatch.
- An 80Mhz common-mode signal will be present on the bus, with levels 1.0mA and 1.8mA.
- Common-mode voltage waveform depends on the local common-mode line impedance and on common-mode reflections off of the terminator.

110011001100
differential waveform

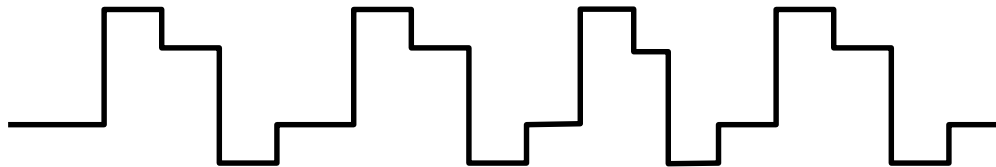


110011001100
Common mode
waveform



- **A 68 wire cable can have up to 32 wires with identical common mode waveforms.**
- **Common-mode cross-talk is not helped by twisting wires.**
- **EM Radiation is a concern.**
- **At 80MHz a 2 meter cable is an efficient antenna.**

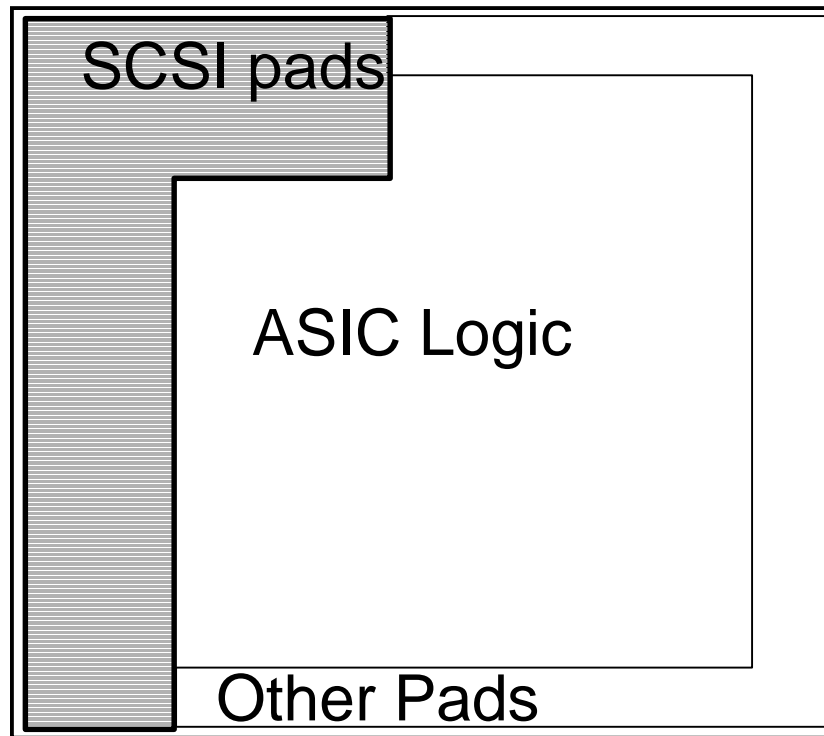- Die area increases
- SCSI pads already a large fraction of ASIC die area




- **Capacitance would increase for an “off” driver**
 - Estimate an increase of 1.2 to 2.5pF to ground on bus- and bus+.
 - Possible problem with 15pF limit in standard for some vendors.
 - Very likely problem with the tighter capacitance limits in some customer purchase specs for most vendors.
 - Backward compatibility problem (Fast-40 or Fast-80) for back-planes which were marginal with current generation drives.
 - More capacitance would invalidate all eye-diagram data taken to date.
- **Some back-plane impedance would drop below 85 Ω with added capacitance.**



- **Chip heating will be greater as average drive power is increased.**
- **Power delivered to bus increases by the product of the boost factor (1.5, 1.8, ...) and the transition density (100% for a 101010 pattern).**
- **Larger thermal gradients across die, making line to line timing de-skew less accurate.**
- **Larger delta temperature between first bits in data transfer and those driven after thermal equilibrium is reached.**
- **In SCSI targets, LVD power already over half of die power.**
- **More elaborate thermal management on target PCBs?**
- **Added power in the pad ring will undermine the chip's timing performance.**

- When LVD drivers are enabled on the bus, it takes over a millisecond to reach thermal equilibrium.
- Driver temperature also depends on adjacent heat sources (other enabled drivers).
- The temperature difference between REQ/ACK and Data will change over time.

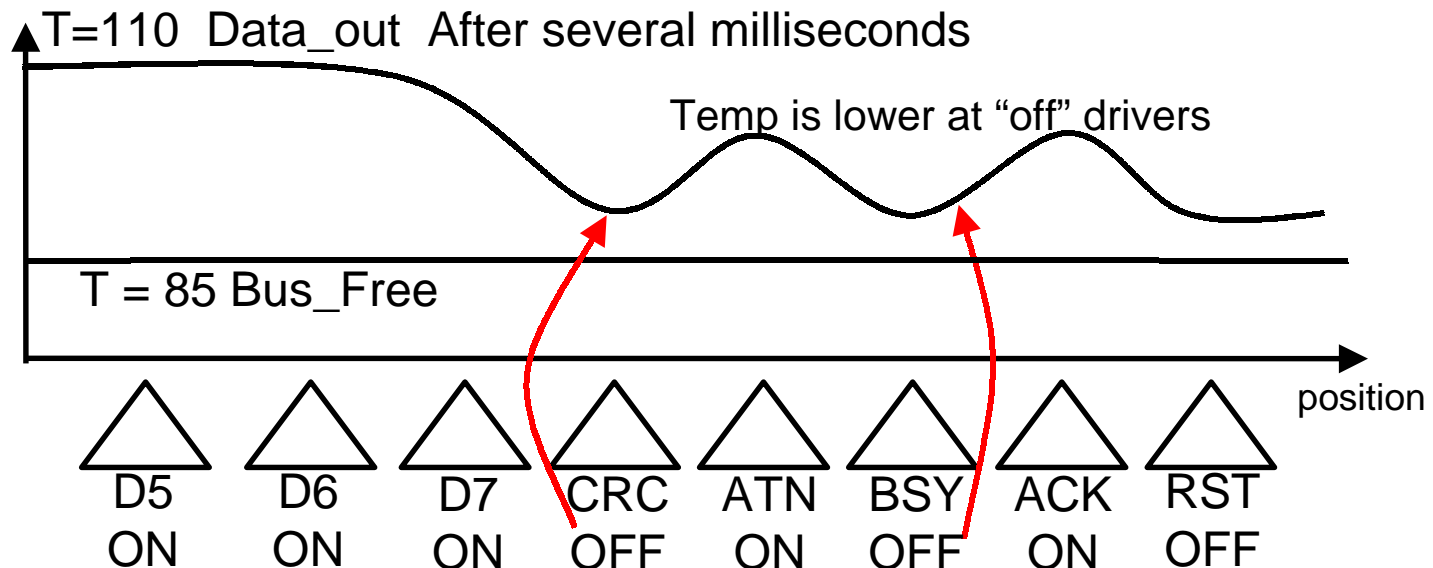Thermal profile of driver output stages parallel to die edge



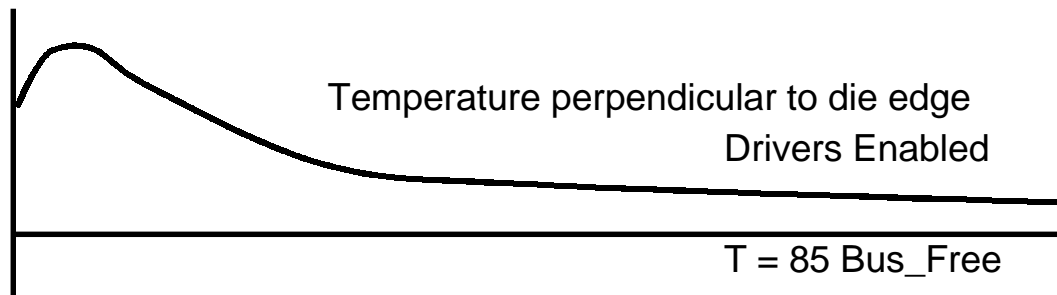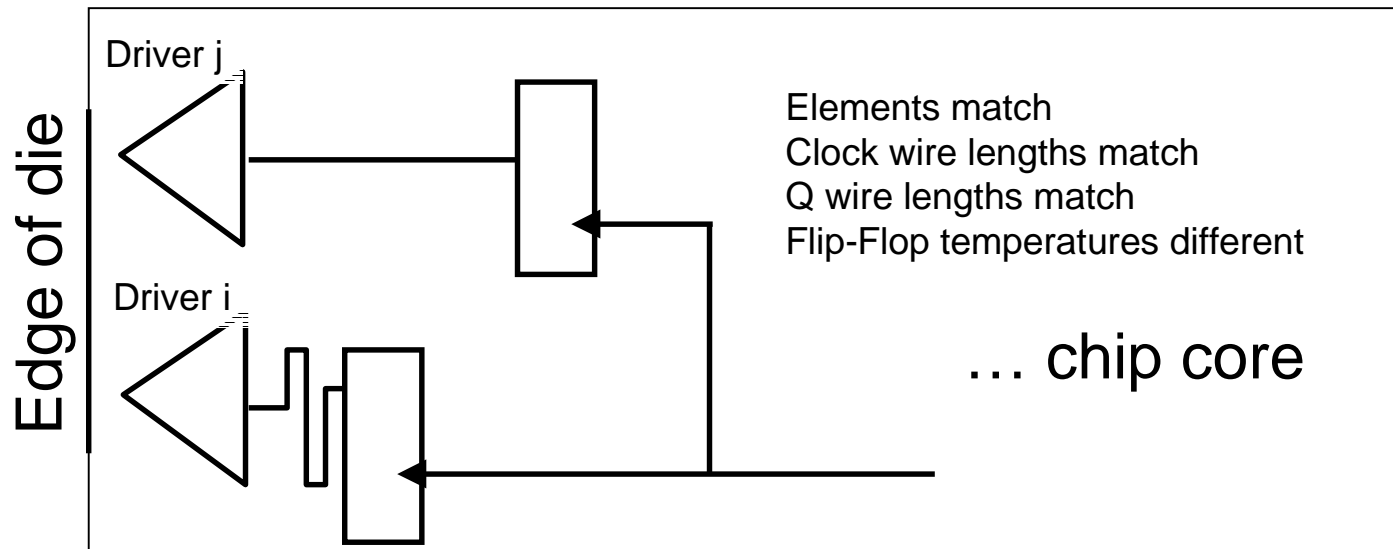
- CAD tools cannot cope with elements at different temperatures.
- Adding more heat to the pad ring makes timing optimization harder.



- **The higher swings must be obtained with the same rise and fall times as in U160 products.**
- **Higher slew rates result, and will result in increased ringing at the transmitter.**
- **Higher slew rates will increase the number of stubs which cause problem reflections.**
- **Currently, any misalignment of pull-up and pull-down pre-drivers leads to a common-mode glitch during a data transition. With a “boost driver”, there are 4 pre-drivers to align instead of the current 2 pre-drivers.**
- **Sensitivity of common mode transition noise to the ASIC chip package and board mismatches (between bus+ and bus-) will increase.**

- **Near End Cross-Talk (NEXT) will increase due to the greater $\partial i / \partial t$ on the driven wire pairs.**
- **Far End Cross-Talk (FEXT) will increase due to the larger voltage swings being driven.**
- **Ratio of coupled cross talk signal to quiescent signal will increase by the boost ratio.**
- **Increased intra-chip coupling through power and ground rails from non-constant current driver.**

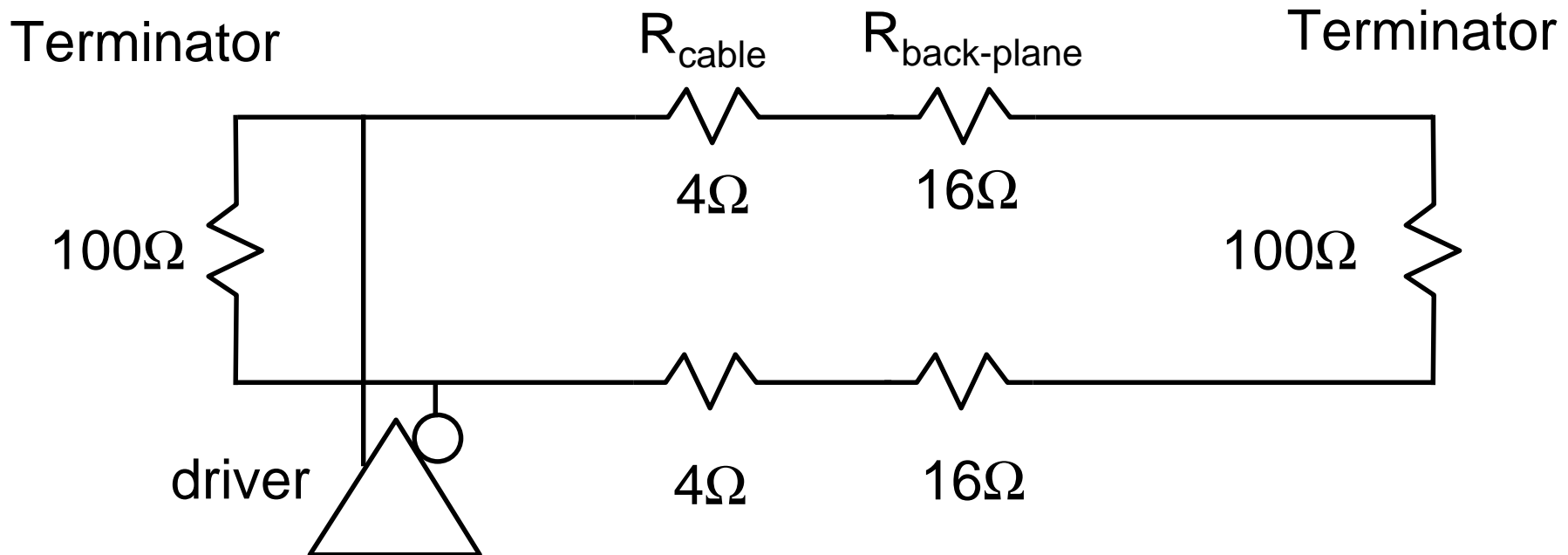- Worst case buses have substantial series resistance.
- Net load R is 58 Ω .
- Adding 1.0mA to driver, adds 58mV to driver (cross-talk source)
- Adding 1.0mA to driver adds only 41mV at far terminator.
- Adding energy at the transmitter is inefficient.



- ① **Current source non-linearity versus drive current.**
- ② **Added common mode signals and noise.**
- ③ **EM radiation issues.**
- ④ **Limits for cables with substantial in-phase common mode signal.**
- ⑤ **Additional capacitance needed.**
- ⑥ **Power increases resulting in increases in local junction temperatures.**
- ⑦ **Temperature profile issues relative to timing budget.**
- ⑧ **Optimal transmitter pre-comp drive levels not yet determined.**
- ⑨ **No proposals yet for transmitter pre-comp algorithms.**

- ① A transmitter pre-comp design which helps ISI without causing significant new problems is not trivial.**
- ② The high multipliers (1.5x - 1.8x) are a major departure from existing LVD technology, and add a lot of risk to U320.**
- ③ Side effects of high ratio transmitter pre-comp will cause problems with backward compatibility and multi-vendor interoperability.**
- ④ We should consider other alternatives.**